



# Bi-Directional Logic Level Converter Hookup Guide

CONTRIBUTORS:  JIMBO


♥ FAVORITE

4
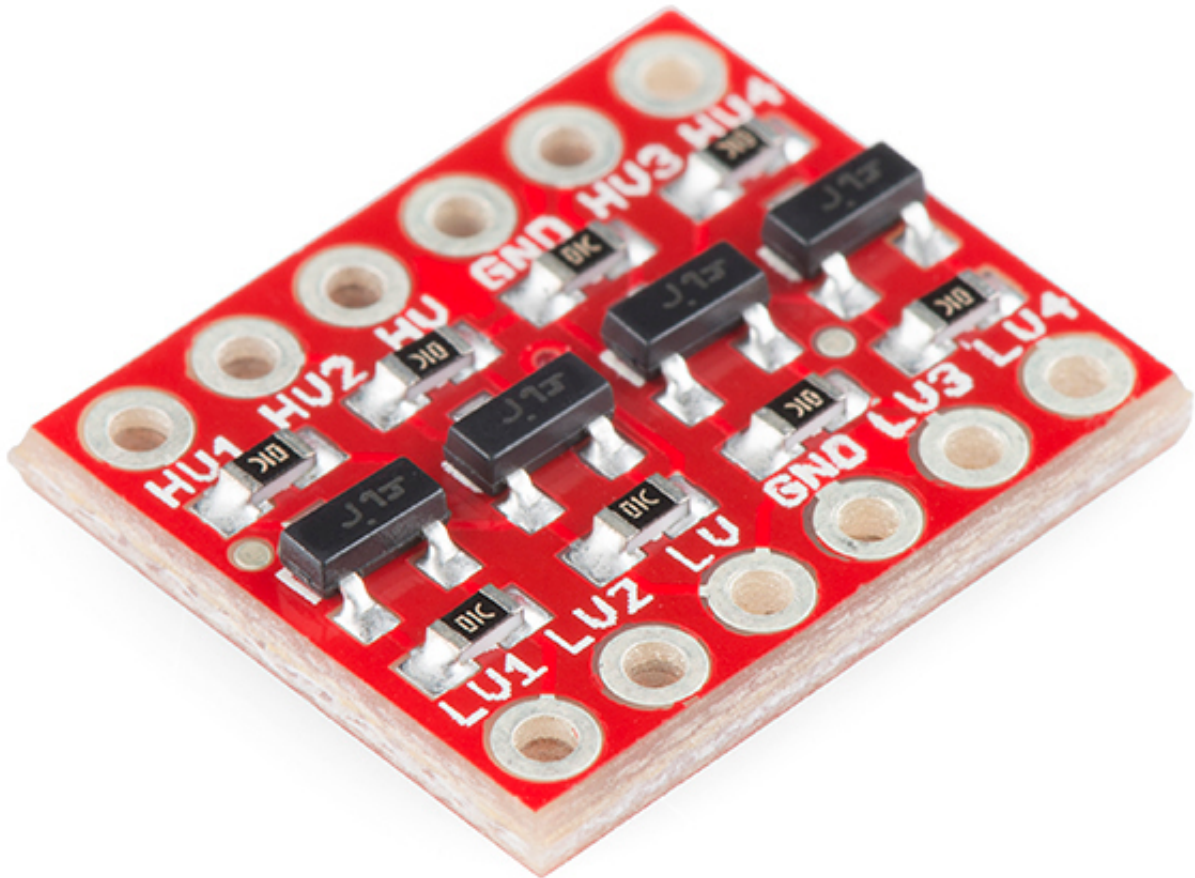
## Introduction

Do you have a 3.3V I<sup>2</sup>C or SPI sensor that might go up in smoke if connected to a 5V Arduino? Or a 5V device that needs a workaround to be compatible with your 3.3V Raspberry Pi, Arduino Due or pcDuino?

To get over this obstacle you need a device that can shift 3.3V up to 5V or 5V down to 3.3V. This is called logic level shifting. Level shifting is a dilemma so common we designed a simple PCB assembly to make interfacing devices a little easier: the Bi-Directional Logic Level Converter.



Though they share the same shape and size, this bi-directional logic level converter shouldn't be confused with the more "uni-directional" version. This converter can pass data from high to low *and/or* low to high on **all channels**. It's perfect for level-shifting between devices that are sharing a data wire, like I<sup>2</sup>C or a one-wire interface.

## Covered In This Tutorial

In this tutorial we'll take an in-depth look at the Bi-Directional Logic Level Converter. We'll examine the schematic and board layout – explaining what each pin on the board does. At the end we'll go over some hookup examples to show how you might hook the board up for various interfaces.

## Suggested Reading

- [Logic Levels](#)
- [How to Use a Breadboard](#)
- [What is an Arduino?](#)
- [How to Solder](#)
- [Working with Wire](#)

---

[← PREVIOUS PAGE](#)[VIEW AS A SINGLE PAGE](#)[NEXT PAGE →  
BOARD OVERVIEW](#)